


Digital Design

Gade Sreehas
ID: 202217B2052

What is Comparator?

A **comparator** takes two numbers as input in binary form and determines whether one number is greater than, less than or equal to the other number.

Simple Comparator

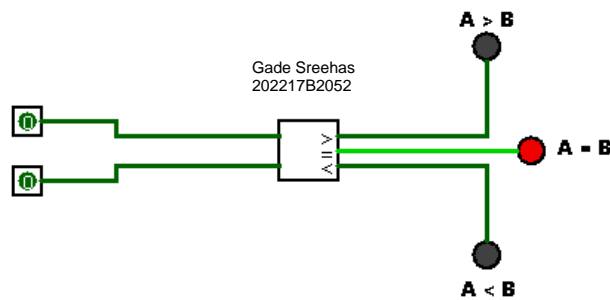

4-bit Comparator with Gates:

Let's consider 2 inputs A, B of 4 bit each.

$A \rightarrow A_3, A_2, A_1, A_0$

$B \rightarrow B_3, B_2, B_1, B_0$

where A_3, B_3 is MSB and A_0, B_0 is the LSB.

Inputs A and B are equal if the corresponding bit of each input are equal i.e.

$A_3 = B_3, A_2 = B_2, A_1 = B_1$ and $A_0 = B_0$

2 bits are equal if the output of their XNOR is 1.

$$X_i = A_i B_i + A_i' B_i' = (A_i B_i' + A_i' B_i)'$$

XNOR Truth Table

| A | B | X |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

1) A = B

Inputs A and B will be equal when $A_3 = B_3, A_2 = B_2, A_1 = B_1$ and $A_0 = B_0$

$$X_i = (A_i B_i' + A_i' B_i)'$$

Output: $X_3 X_2 X_1 X_0$

2) A > B

Input A will be greater than B when iff

$A_3 = 1$ and $B_3 = 0$ (or)

$A_3 = B_3$ and $A_2 = 1$ and $B_2 = 0$ (or)

$A_3 = B_3, A_2 = B_2$ and $A_1 = 1$ and $B_1 = 0$ (or)

$A_3 = B_3, A_2 = B_2, A_1 = B_1$ and $A_0 = 1$ and $B_0 = 0$

Output: $A_3 B_3' + X_3 A_2 B_2' + X_3 X_2 A_1 B_1' + X_3 X_2 X_1 A_0 B_0'$

3) A < B

Input A will be lesser than B when iff

$A_3 = 0$ and $B_3 = 1$ (or)

$A_3 = B_3$ and $A_2 = 0$ and $B_2 = 1$ (or)

$A_3 = B_3, A_2 = B_2$ and $A_1 = 0$ and $B_1 = 1$ (or)

$A_3 = B_3, A_2 = B_2, A_1 = B_1$ and $A_0 = 0$ and $B_0 = 1$

Output: $A_3' B_3 + X_3 A_2' B_2 + X_3 X_2 A_1' B_1 + X_3 X_2 X_1 A_0' B_0$

The truth table for a 4-bit comparator


| Comparing Inputs | | | | Outputs | | |
|------------------|-------------|-------------|-------------|---------|---------|---------|
| A_3B_3 | A_2B_2 | A_1B_1 | A_0B_0 | $A > B$ | $A < B$ | $A = B$ |
| $A_3 > B_3$ | x | x | x | 1 | 0 | 0 |
| $A_3 < B_3$ | x | x | x | 0 | 1 | 0 |
| $A_3 = B_3$ | $A_2 > B_2$ | x | x | 1 | 0 | 0 |
| $A_3 = B_3$ | $A_2 < B_2$ | x | x | 0 | 1 | 0 |
| $A_3 = B_3$ | $A_2 = B_2$ | $A_1 > B_1$ | x | 1 | 0 | 0 |
| $A_3 = B_3$ | $A_2 = B_2$ | $A_1 < B_1$ | x | 0 | 1 | 0 |
| $A_3 = B_3$ | $A_2 = B_2$ | $A_1 = B_1$ | $A_0 > B_0$ | 1 | 0 | 0 |
| $A_3 = B_3$ | $A_2 = B_2$ | $A_1 = B_1$ | $A_0 < B_0$ | 0 | 1 | 0 |
| $A_3 = B_3$ | $A_2 = B_2$ | $A_1 = B_1$ | $A_0 = B_0$ | 0 | 0 | 1 |

In the above table 0 = Low Voltage level, 1 = High Voltage level and x = Don't Care

Circuit Components: -


1. 8 data inputs of 1 – bits: – $A_3, A_2, A_1, A_0, B_3, B_2, B_1, B_0$
2. To Implementing XNOR for 8 bits we require 12 NOT gates, 8 AND gates and 4 OR gates.
3. 1 AND gate of 4 inputs is required for output " $A = B$ "
4. 3 AND gates and 1 OR gates of 4 inputs are required for output " $A > B$ "
5. 3 AND gates and 1 OR gates of 4 inputs are required for output " $A < B$ "

Labeling equation for comparator: -

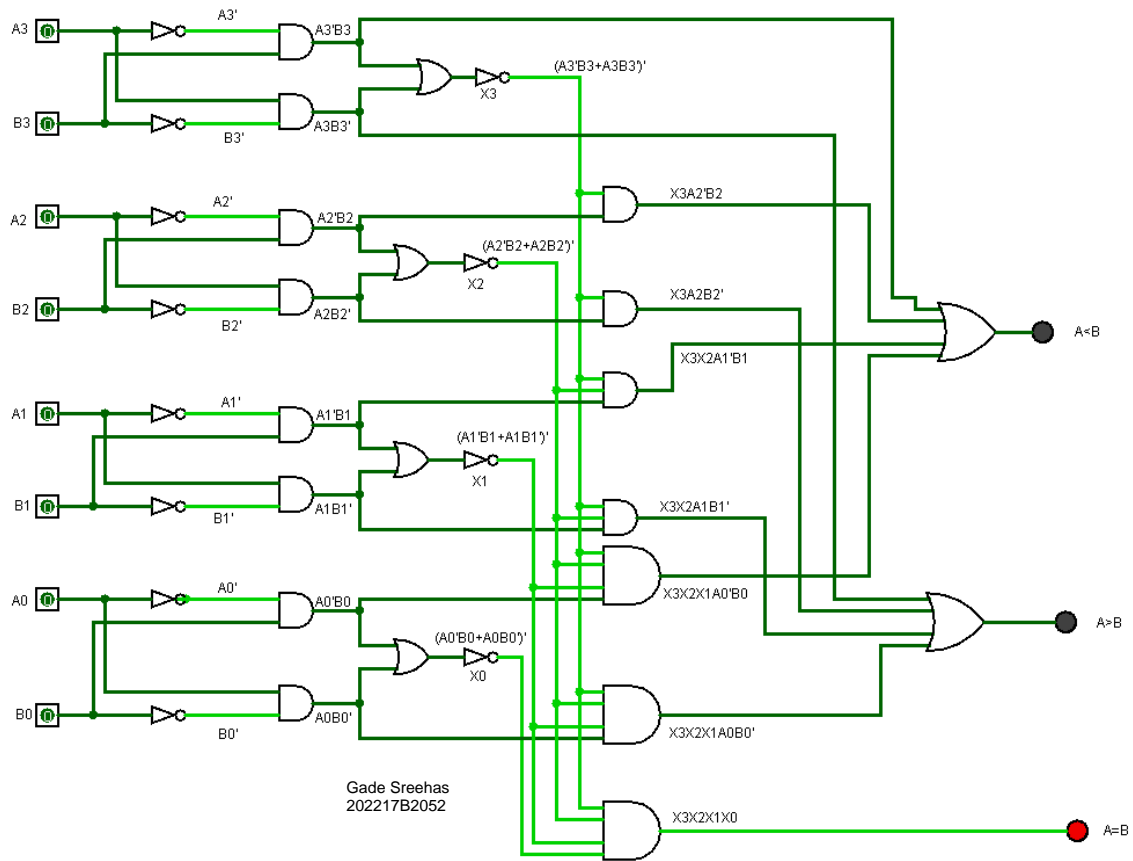


For,

1) $A = B$

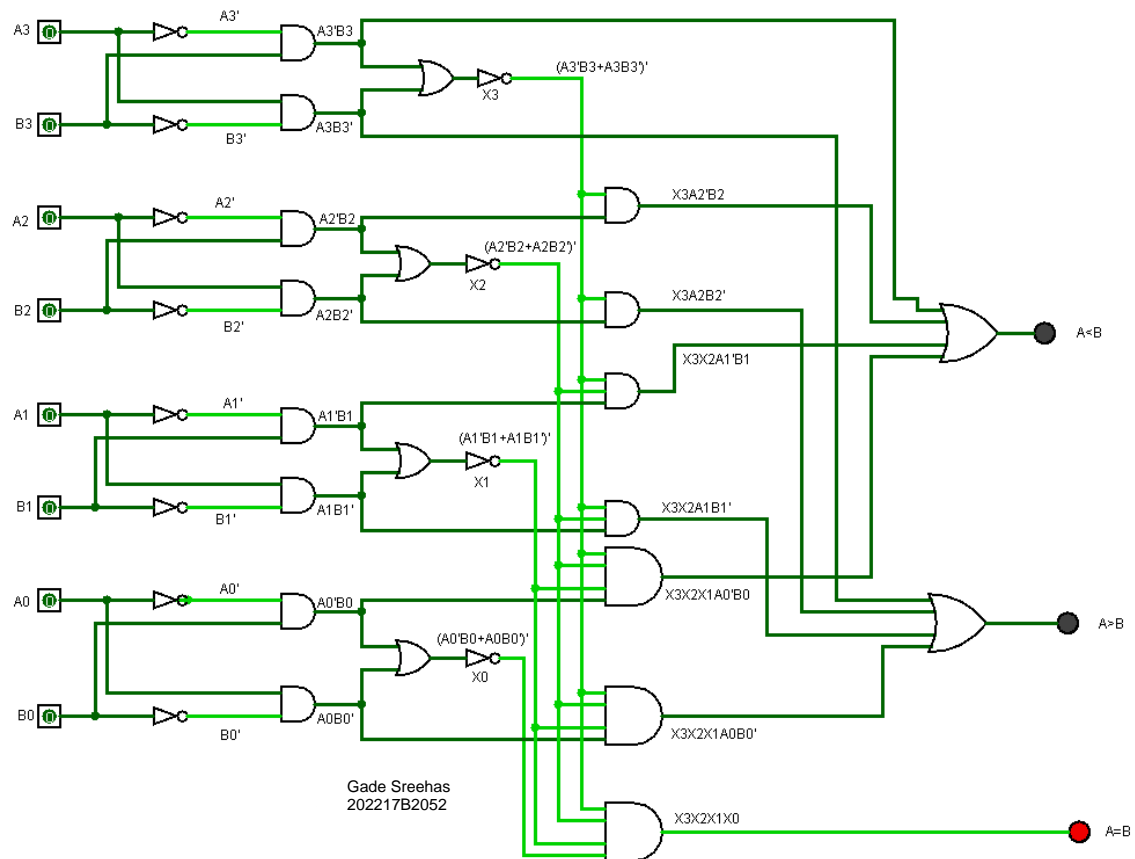

2) $A > B$

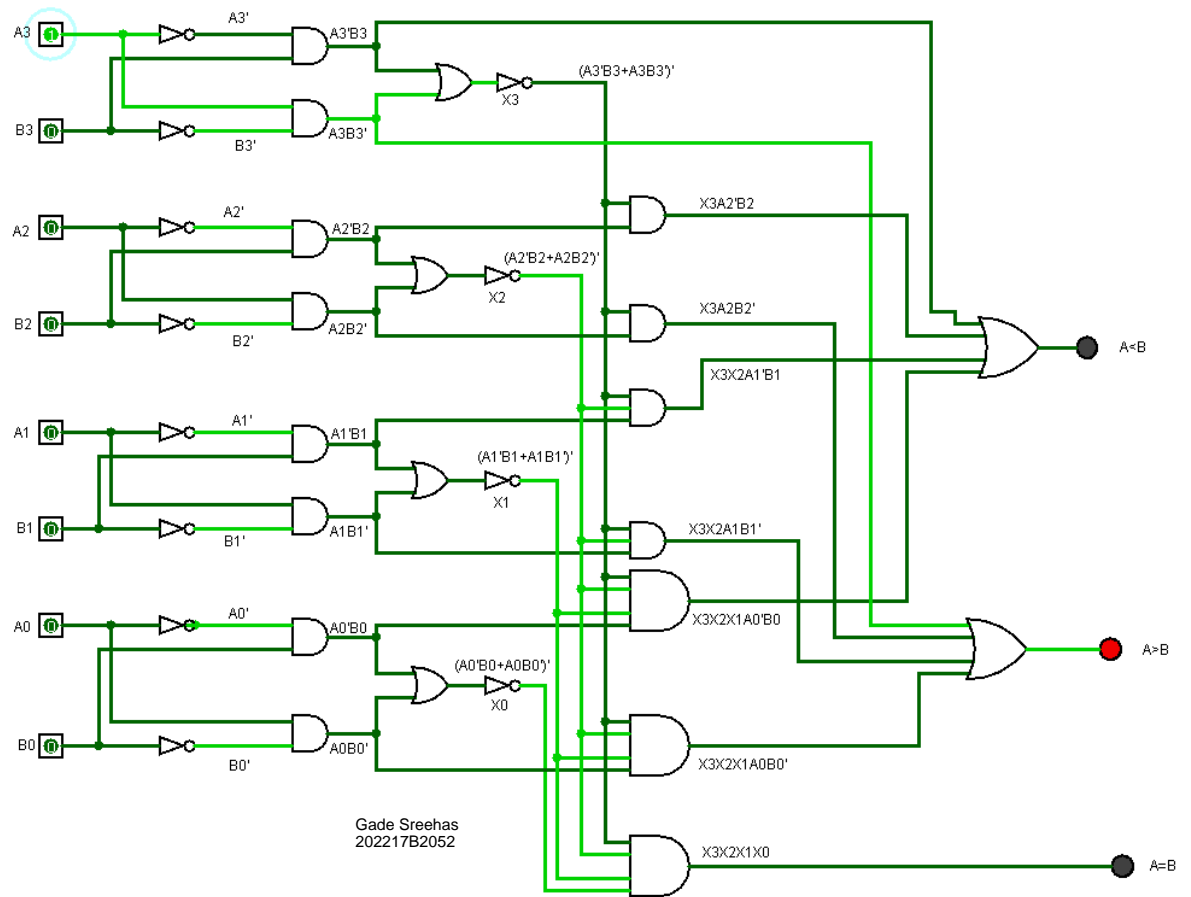

3) $A < B$

